

Learning engineering to teach mathematics

January 2010
San Francisco

Josep FERRER*, Carmen ORTIZ**, Marta PEÑA*

*Universitat Politècnica de Catalunya (Spain)

**Universidad de Extremadura (Spain)

Seminar of mathematics for engineering

Introduce examples of engineering use
to increase students interest at learning mathematics.

Electrical
Engineering

Optimization
and Simulation

Mechanical
Engineering

Elasticity and
Materials'
Resistance

Automatics
and Control

In the following slides a brief introduction to **electrical engineering** will be carried out as an example of the information collected during the seminar:

- Guideline for teachers
- Exercises for students

Circuit analysis

Study of the system of equations derived from the Ohm's and Kirchoff's laws

Circuit analysis

Circuit

- M meshes with N nodes and B branches.

Objective

- Determine **currents** and **tensions** distribution (i_k, u_k) , $1 \leq k \leq B$.

Tools

- Ohm's law: $u_k = R_k i_k + e_k$, each branch where e_k is the generated tension
- Kirchoffs' law: $\sum u_k = 0$, in each node
and $\sum i_k = 0$, in each mesh

Circuit analysis

STEP 1

- Ohm's law establishes an **isomorphism between currents and tensions** so that we just need to refer to one of both variables

$$\text{(KCL)} \quad \sum i_k = 0 \quad \text{in each node.}$$

$$\text{(KVL)} \quad \sum R_k i_k = -\sum e_k \quad \text{in each mesh.}$$

STEP 2

- **One node equations is redundant** so that we have $N+M-1=B$ equations with B unknowns.
- It is a **consistent determined system** because so it is its homogeneous associate (if $e_k=0$, there is not energy contribution, meaning that the currents will turn to be null).


STEP 3

- Therefore:
 $\dim \{solutions\ KCL\} = B - (N-1) = M$
- **The mesh currents are linearly independent.** Then, they are a basis of this subspace

Circuit analysis

EXERCISE 1 DIMENSION AND BASIS OF THE SUBSPACE OF SOLUTIONS OF KLC

Consider the following mesh

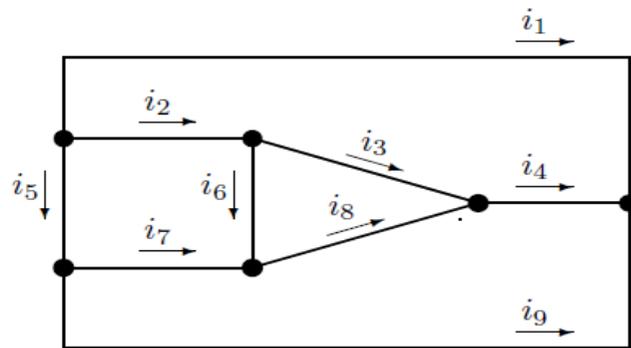


Being E the set of possible current's distributions, find out the subset verifying the Kirchoff's law

$$\sum i_k = 0$$

Prove that it is a subspace parametrized by the mesh currents.

MESH CURRENTS

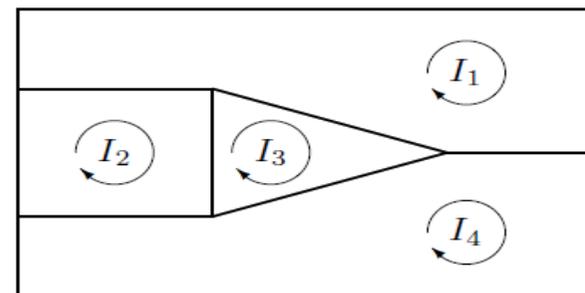

Alternating currents

Use of complex numbers
as representation of
electrical magnitudes for
alternating currents

Alternating currents

Direct current
representation

- Set of Real numbers

Generalization

Alternating current
representation

- Set of Complex numbers

Reality

Cosenoidal

$$m(t) = \sqrt{2}M \cos(\omega t + \alpha)$$

M : **root mean square** value (rms)

α : **phase angle**

ω : **frequency** (constant)

Representation

Fasorial

$$\underline{M} = Me^{i\alpha}$$

Alternating currents

Kirchoff's laws (linear correspondence)

- (KVL) $\sum \underline{I}_k = 0$ in each node.
- (KCL) $\sum \underline{U}_k = 0$ in each mesh.

Ohm's law (field structure):


- $\frac{\underline{U}_k}{\underline{I}_k} = \underline{Z}_k$ \underline{Z}_k is the impedance.
- Thanks to $m'(t) = j\omega m(t)$ it includes
 - Resistance case $u(t) = Ri(t)$ $\underline{U} = R\underline{I}$
 - Condenser case $i(t) = Cu'(t)$ $\underline{I} = j\omega C\underline{U}$
 - Coil case $u(t) = Li'(t)$ $\underline{U} = j\omega L\underline{I}$

Alternating currents

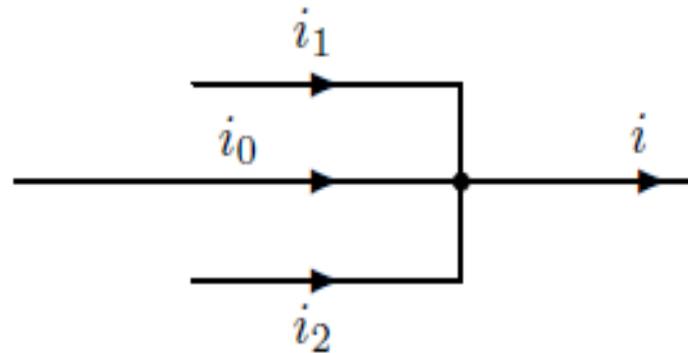EXERCISE 2 KLC FOR ALTERNATING CURRENTS

Calculate the current resultant of incrementing it with two others of 75% and 50% of rms, shifted 120° and 90° respectively

$$i_1(t) = 0.75\sqrt{2}I_0 \cos\left(\omega t + \frac{\pi}{3}\right) \quad i_2(t) = 0.50\sqrt{2}I_0 \cos\left(\omega t + \frac{\pi}{4}\right)$$




Alternating currents

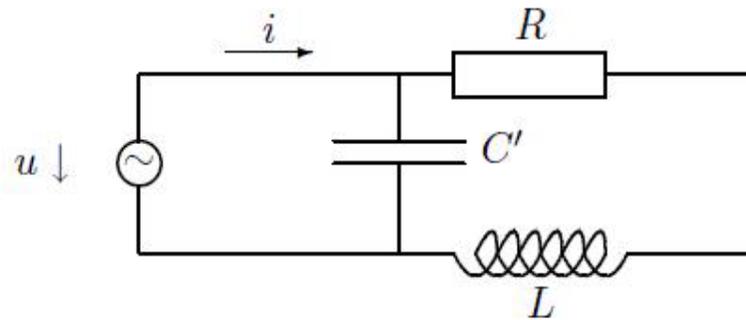EXERCISE 3 PARALLEL RESONANCE

Prove for the circuit that the impedance is real if only if

$$\omega L = \sqrt{\frac{L}{C} - R^2} \quad \text{and then} \quad Z = \frac{L}{RC}.$$



Magnetic couplers

Circulant matrices
appearing as magnetic
couplers of some type of
motors and inductance
machinery

Magnetic couplers

- Inductance operator (particular case from the matrix called circulant):

$$Z = \begin{pmatrix} c_1 & c_2 & c_3 \\ c_3 & c_1 & c_2 \\ c_2 & c_3 & c_1 \end{pmatrix} \in M_3(\mathbb{C})$$

- The following statements are equivalent:
 - Z is a circulant matrix
 - Z diagonalized by orthogonal transformation

$$F = \frac{1}{\sqrt{3}} \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \quad a = e^{j\frac{2\pi}{3}}$$

- If A and B are circulant matrices, the matrices $A+B$ and AB are also circulant, and their eigenvalues are the sum and product, respectively, of those of A and B .
- From a technical point of view, the eigenvalues give the decomposition on monophasics.

Magnetic couplers

EXERCISE 4 EIGENVECTORS OF A CIRCULANT MATRIX

Prove that any circulant matrix

$$A = \begin{pmatrix} a & b & c \\ c & a & b \\ b & c & a \end{pmatrix} \quad a, b, c \in \mathbb{C}$$

diagonalizes with the transformation S

$$S = \begin{pmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{pmatrix} \quad \alpha^3 = 1$$

Calculate the diagonal form.